

1. State and prove DeMorgan's theorem and expand the function: $(A+B'+C+D')' + (ABCD)'$.
2. Simplify the Boolean function using K-map methods.

$$F(A, B, C, D) = m(4, 5, 6, 7, 8)$$

$$d(A, B, C, D) = m(11, 12, 13, 14, 15)$$

3. What is the minimum number of 2-input NAND gates required to implement a 4-variable function expressed in sum-of-minterms form as $f = (0, 2, 5, 7, 8, 10, 13, 15)$?
4. Draw and explain the logic diagram of a half adder using only NAND gates.
5. Evaluate the 2's complement of decimal 28.
6. Convert the following:

$$(145.21)_{10} \rightarrow (X)_{16}$$

$$(AB9)_{16} \rightarrow (x)_8$$

$$(176.23)_{10} \rightarrow (x)_8$$

$$(36.89)_{10} \rightarrow (x)_4$$

$$(10AE)_{16} \rightarrow (X)_8$$

$$(7.75)_8 \rightarrow (x)_2$$

7. Minimize the following:

$$Z = \sum A, B, C(0, 4, 5)$$

$$Z = \sum A, B, C(1, 5, 6, 7, 9, 13)$$

$$Y = AB'C + A'B'C + A'BC + AB'C' + A'B'C'$$

$$F = A' + AB' + ABC'$$

$$Y = ABC'D + ABC'D' + ABCD + A'BCD + ABCD' + A'BCD'$$

$$Y(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 7, 8, 9, 10, 11, 12, 14)$$

$$Y = (A' + B' + C + D)(A + B' + C + D)(A + B + C + D')(A + B + C' + D')(A' + B + C + D')(A + B + C' + D)$$

8. Design 8x1 Multiplexer using 4x1 Multiplexer and 2x1 Multiplexer.

9. Design 3 to 8 decoder using 2 to 4 decoders.
10. Design Mod-10 Counter.